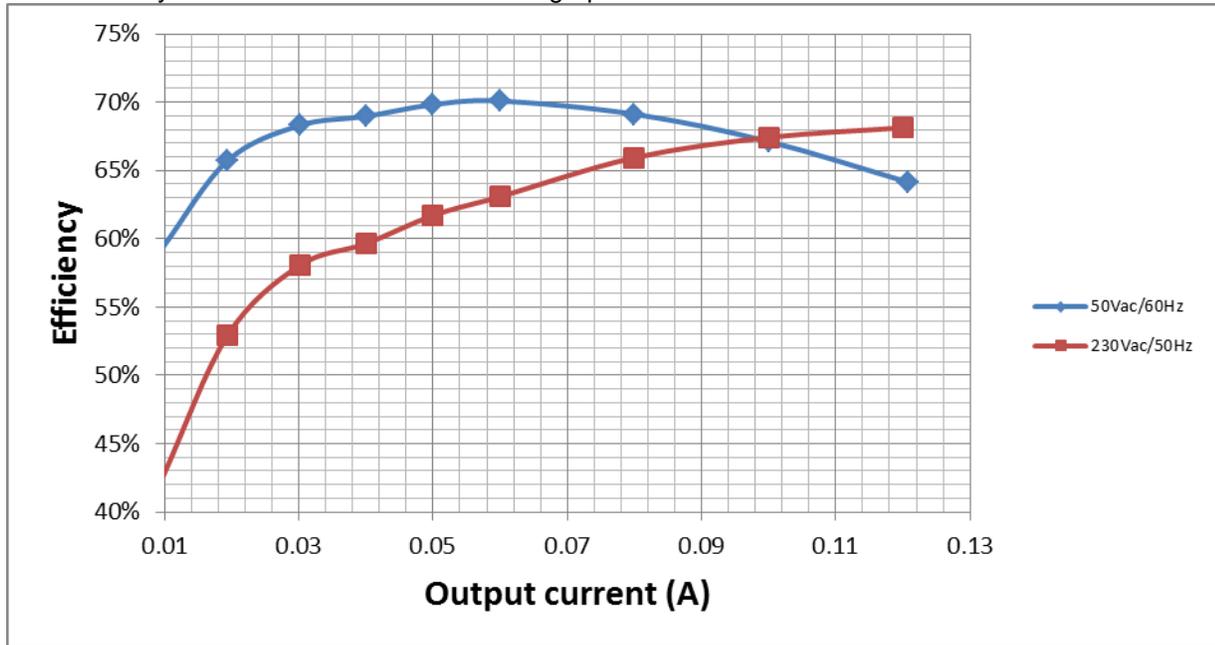


2 Converter Efficiency

The efficiency data is shown in the tables and graph below.



V_{in}=50V_{AC}/60Hz

V _{in} (V)	I _{in} (mA)	P _{in} (W)	V _{out} (V)	I _{out} (A)	P _{out} (W)	Losses(W)	Efficiency (%)
50.04	75.81	1.725	9.16	0.1208	1.106528	0.618472	64.15%
50	59.94	1.363	9.15	0.1	0.915	0.448	67.13%
50.02	47.45	1.06	9.16	0.08	0.7328	0.3272	69.13%
50.04	36.28	0.7841	9.16	0.06	0.5496	0.2345	70.09%
50.07	31.04	0.6566	9.17	0.05	0.4585	0.1981	69.83%
50.06	25.83	0.5318	9.17	0.04	0.3668	0.165	68.97%
50.09	20.4	0.404	9.17	0.03009	0.275925	0.1280747	68.30%
50.12	14.45	0.2706	9.19	0.01935	0.177827	0.0927735	65.72%
50.15	8.732	0.15062	9.21	0.00971	0.089429	0.0611909	59.37%
50.18	1.974	0.02795	9.25	0	0	0.02795	0.00%

V_{in}=230V_{AC}/50Hz

Vin(V)	Iin(mA)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
230	22.96	1.613	9.16	0.12	1.0992	0.5138	68.15%
230	19.74	1.357	9.15	0.1	0.915	0.442	67.43%
230	16.543	1.11	9.15	0.08	0.732	0.378	65.95%
230	13.306	0.871	9.16	0.06	0.5496	0.3214	63.10%
230	11.51	0.7429	9.17	0.05	0.4585	0.2844	61.72%
230	9.67	0.6156	9.18	0.04	0.3672	0.2484	59.65%
230	7.598	0.4751	9.16	0.03011	0.275808	0.1992924	58.05%
230	5.386	0.3353	9.16	0.01938	0.177521	0.1577792	52.94%
230	3.247	0.2095	9.17	0.00973	0.089224	0.1202759	42.59%
230	0.7799	0.07597	9.25	0	0	0.07597	0.00%

3 Thermal Images


The thermal images below show a top view and bottom view of the board under 50V_{ac}/60Hz and 230V_{ac}/50Hz input conditions. The ambient temperature was 20°C with no forced air flow. The output was at full load: 9V/0.12A.

V_{in}=50V_{AC}/60Hz

Top Side




Bottom Side

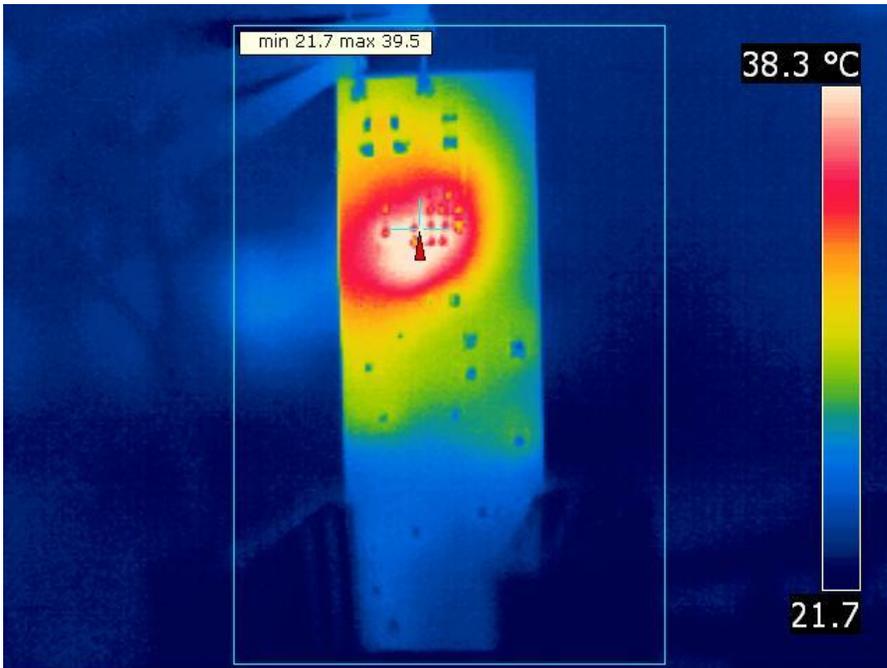

$V_{in}=230V_{AC}/50Hz$
Top Side




Bottom Side

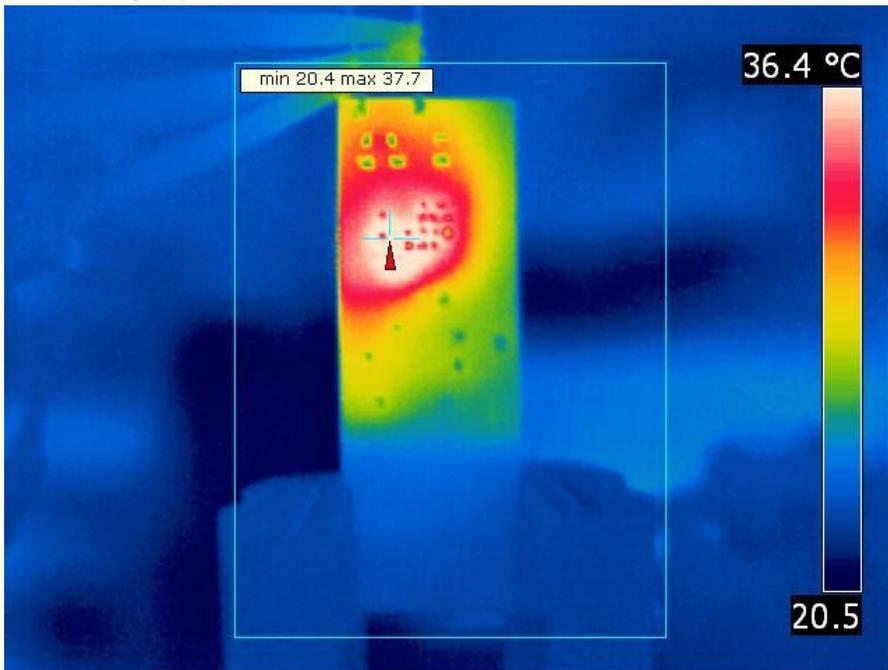

4 Startup Waveforms

The output voltages at startup with constant current load are shown in the images below.


4.1 Start Up @ 50V_{ac}: 9V/0.12A.

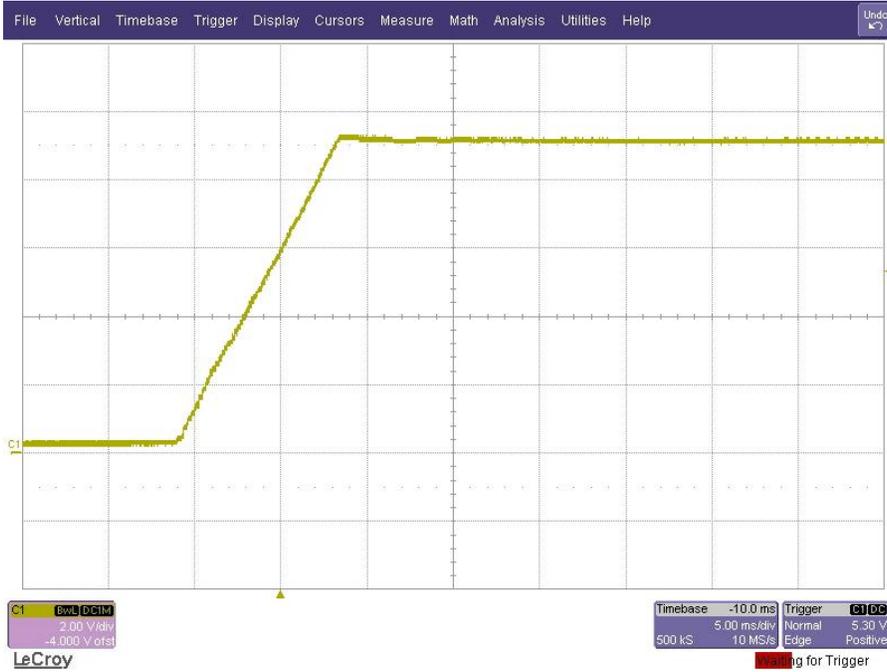

4.2 Start Up @ 50V_{ac}: no load.




4.3 Start Up @ 120V_{ac}: 9V/0.12A.

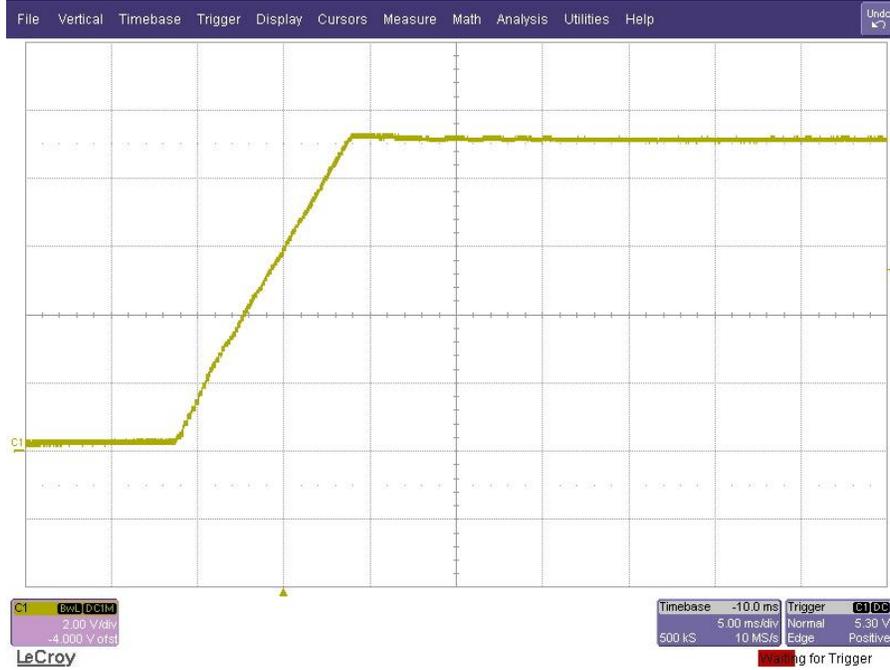


4.4 Start Up @ 120V_{ac}: no load.



4.5 Start Up @ 230V_{ac}: 9V/0.12A.

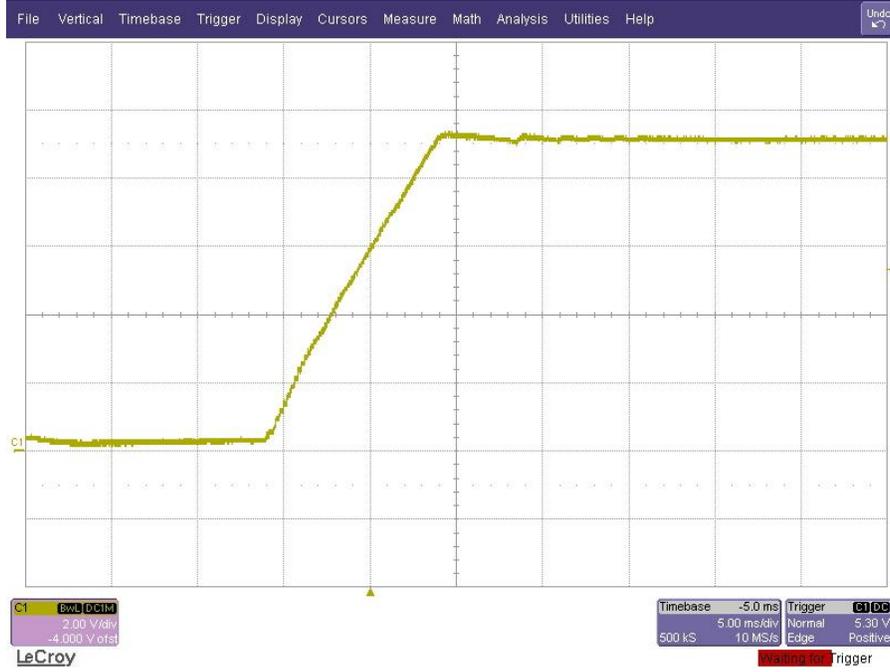


4.6 Start Up @ 230V_{ac}: no load.

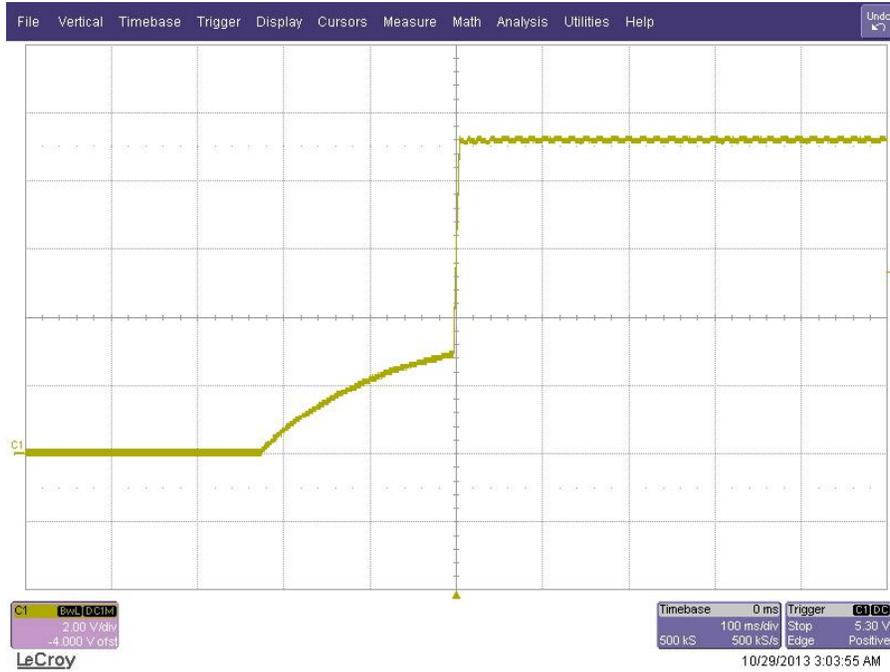

5 Turn off

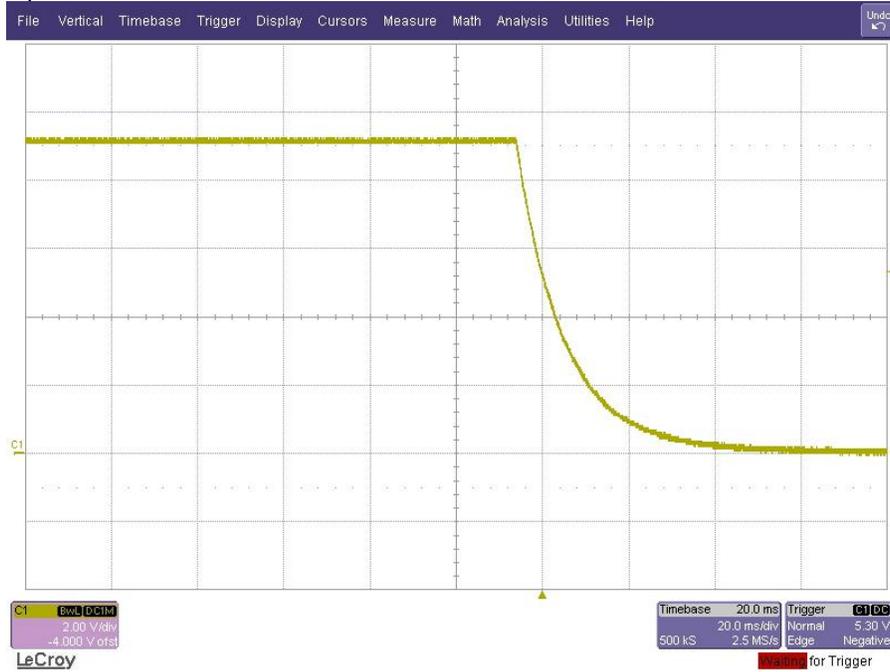
The output voltage at turn off transient is shown in the image below at full load (9V/0.12A) and 120V_{ac}/60Hz input.



6 Output Ripple Voltages

The output ripple voltages are shown in the plots below.


6.1 50V_{ac}: 9V/0.12A.

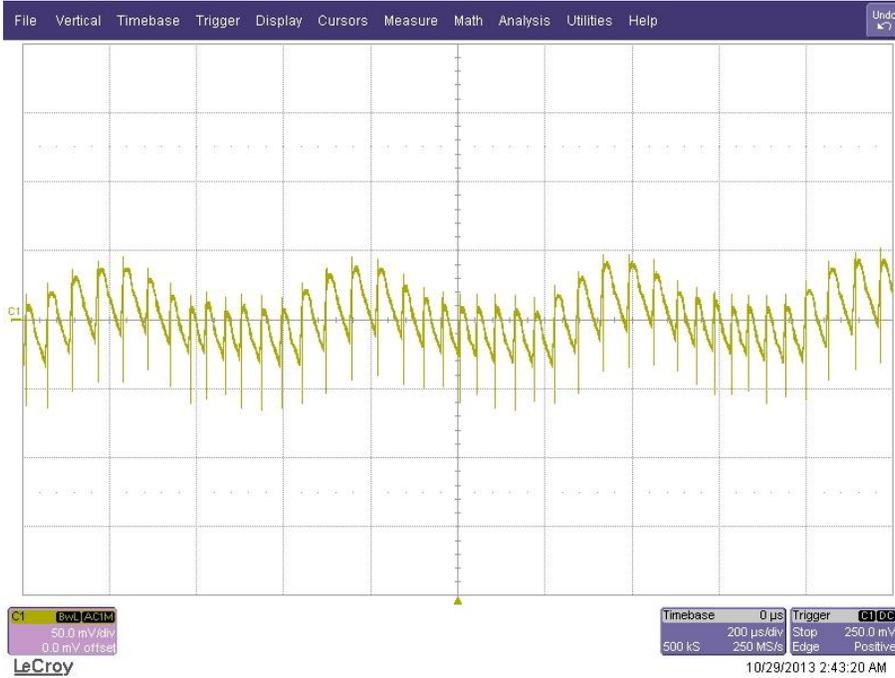

6.2 50V_{ac}: No load.




6.3 120V_{ac}: 9V/0.12A.

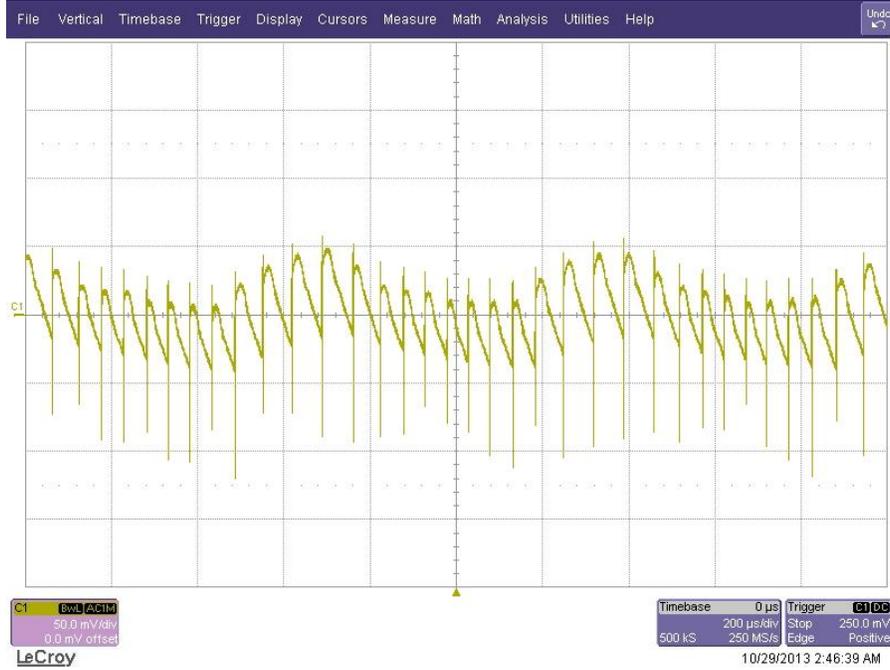


6.4 120V_{ac}: No load.



6.5 230V_{ac}: 9V/0.12A.

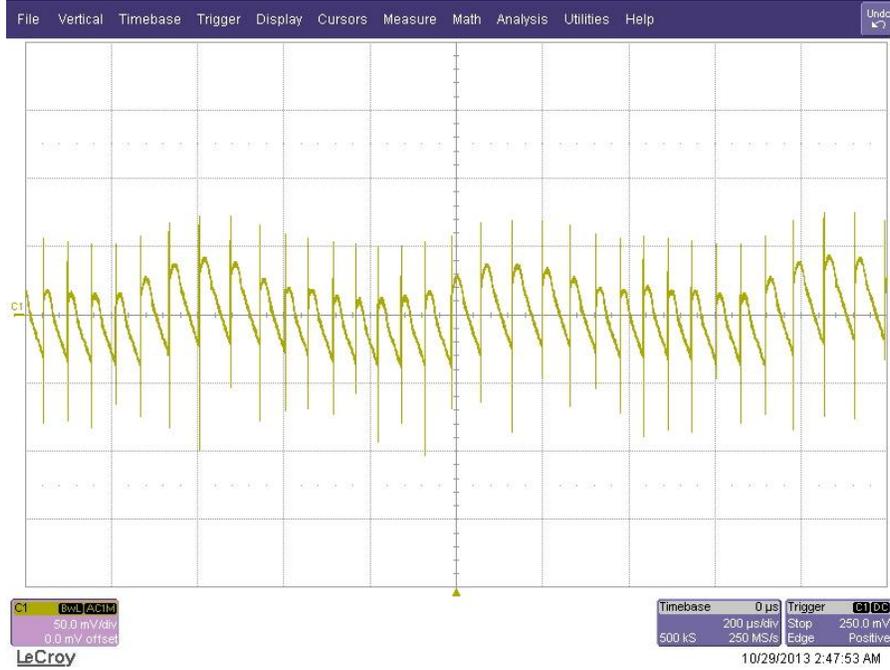


6.6 230V_{ac}: No load.

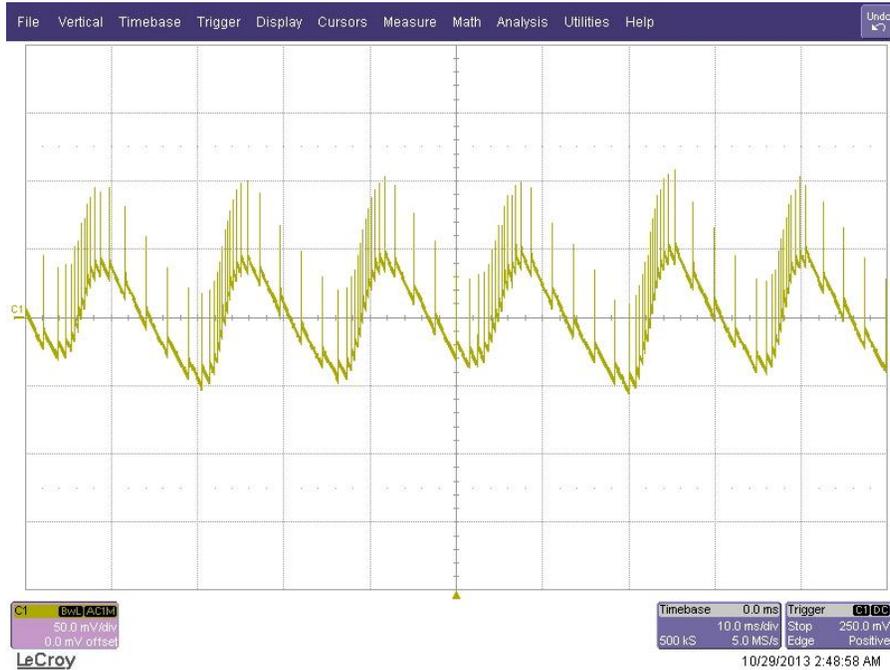

7 Load Transient

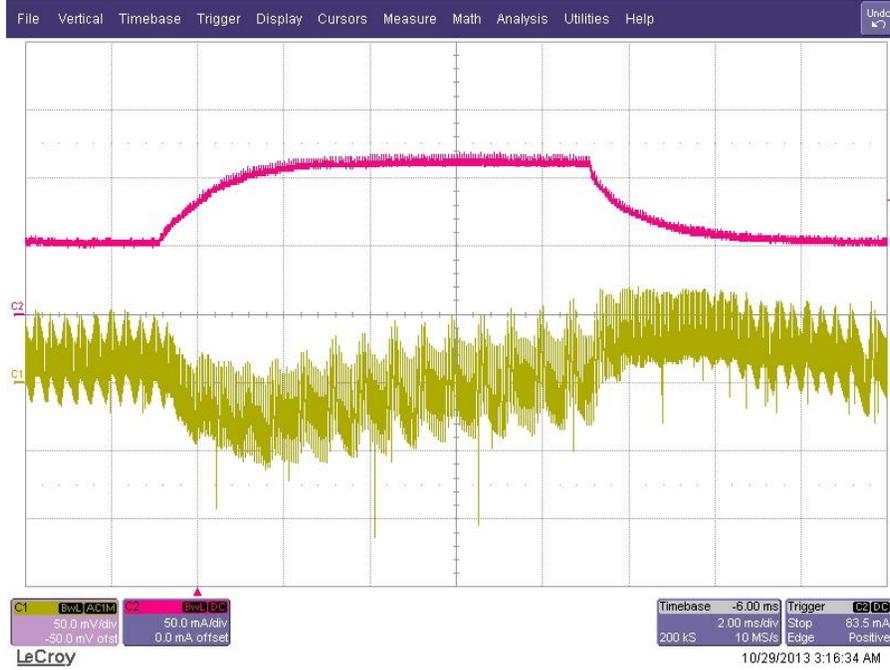
The image below shows $9V_{out}$ voltage response to a **0.06A** to **0.12A** load transient @ $120V_{ac}/60Hz$.




8 Switching Waveforms

The images below show key switching waveforms of PMP9176RevA. The waveforms are measured with 0.12A full load.


8.1 Diode D4 @ 50V_{ac}/60Hz

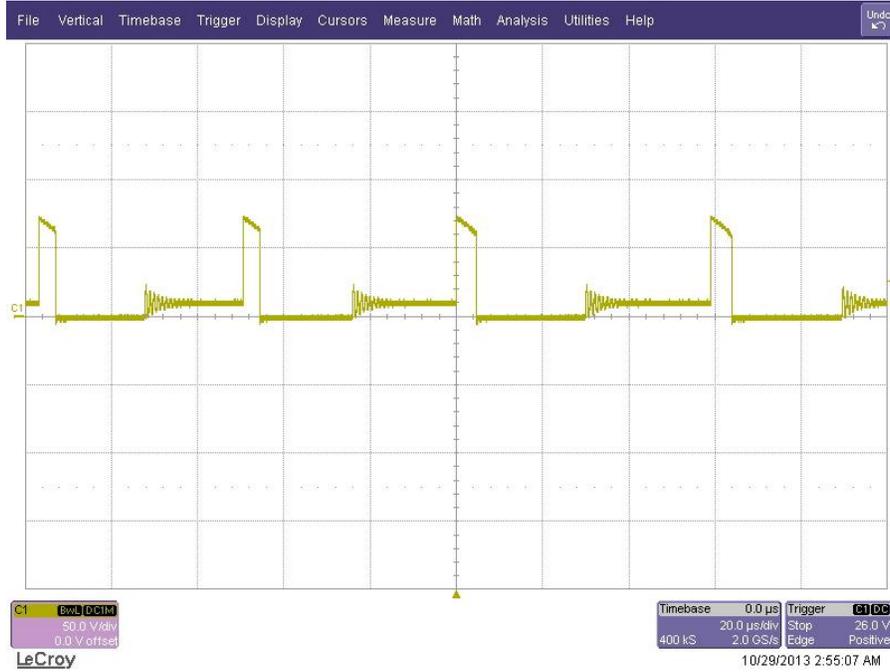


8.2 Diode D4 @ 120V_{ac}/60Hz

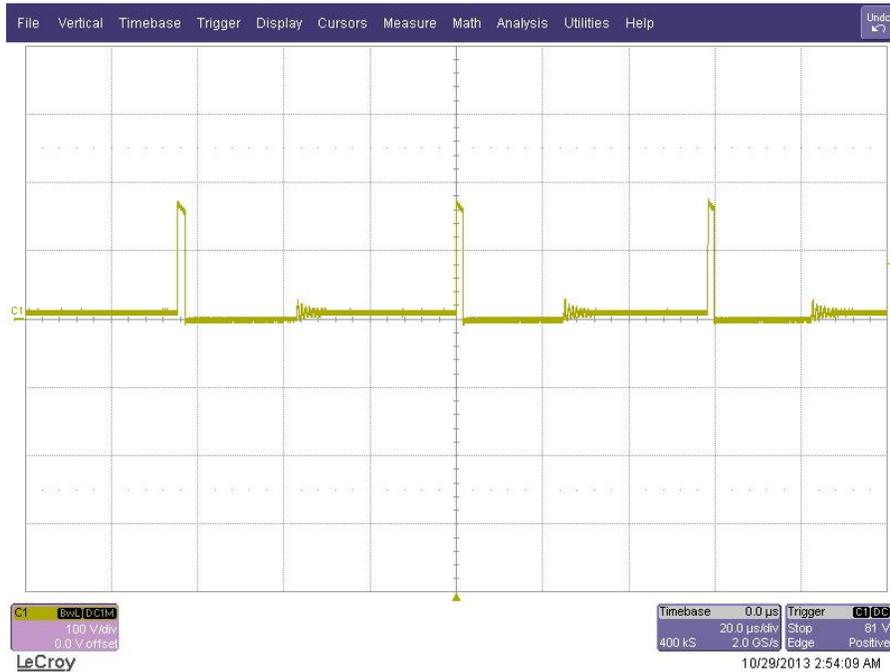

8.3 Diode D4 @ 230V_{ac}/60Hz

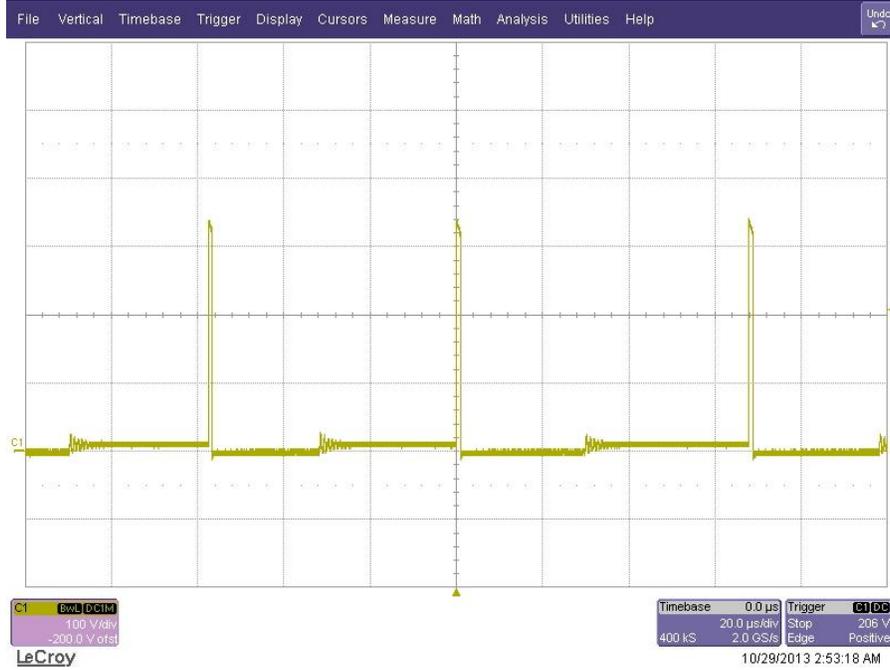

8.4 Diode D4 @ 275V_{ac}/60Hz

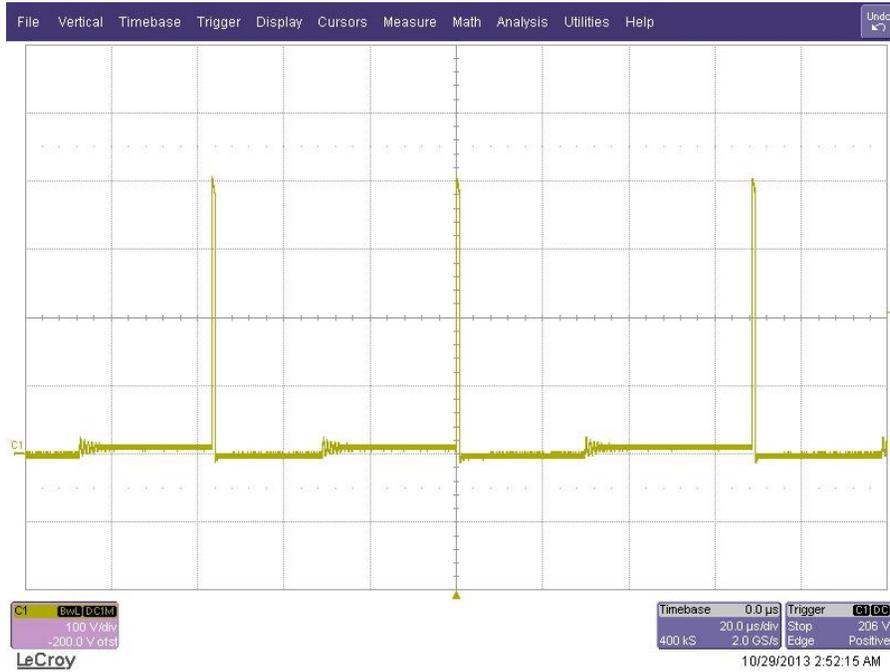

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated