

Using Power IC for OMAP34xx to 36xx Family

ABSTRACT

The OMAP36xx family MPU can operate at up to 1 GHz. These new use cases increase 36xx current requirement. This document describes how to use the power IC with an OMAP36xx at 1 GHz.

This application note is applicable for TPS65921 and TPS65950 devices.

Contents

1	Introduction	1
2	Description of Changes	1
3	Power IC Impact	
	List of Tables	

1	VDD1 Components List for 34xx	1
2	VDD1 Components List for OPP1G	2
3	VDD1 DC-DC Regulator Characteristics	3
4	VDD1 DC-DC Regulator Characteristics	4

1 Introduction

The new OMAP36xx family MPU running at 1 GHz needs more current from VDD1 power supply domain. The rest of the supply tree remains unchanged.

2 Description of Changes

2.1 Application Schematic With OMAP34xx

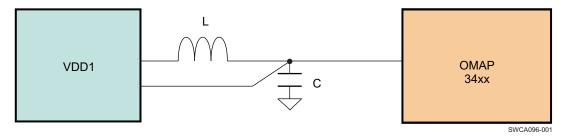


Figure 1. VDD1 External Components Connectivity for OMAP34xx

Component	Min	Min Typical Max		Unit
L	0.7	1	1.3	μH
С	5	10	15	μF

www.ti.com

2.2 Application Schematic With OMAP36xx Running at 1 GHz

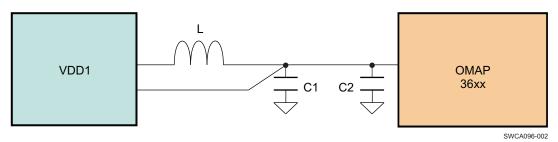


Figure 2. VDD1 External Components Connectivity for OMAP36xx

Component	Min	Typical	Max	Unit
L	0.7	1	1.3	μH
C1	11	22	33	μF
C2	11	22	33	μF

Table 2. VDD1 Components List for OPP1G

2.3 Change List and Points To Check

2.3.1 Inductor Saturation Current

VDD1 current increases; therefore, the inductor saturation increases up to a minimum of 2.1 A. This value must be at the inductor maximum temperature.

NOTE: Inductor DC resistance must be chosen carefully. A resistance which is too high affects DC-DC efficiency.

2.3.2 Voltage Drop from DC-DC Output Sense Point to OMAP Supply Balls

The DC-DC regulates the voltage at the point where the sense line is connected. Therefore, the voltage drop between the sense point and the OMAP[™] MPU balls must be carefully minimized.

2.3.3 Load Transient Improvement

It is possible to improve the load transient. To achieve this, capacitor C1 should be increased to 22 μ F and a capacitor of the same value as C2 can be added close to the OMAP balls. C1 is still located at the sense point.

2.3.4 Power Distribution Network

For simplicity, only tank capacitors are drawn. Some low-value capacitors must be placed along the VDD1 trace to ensure a flat frequency response of the power distribution network (PDN).

2.4 Software Compatibility

The programming model is identical between current devices and devices with enhanced current capability. No software update is necessary.

3 Power IC Impact

3.1 Part Number Upgrade

The part names are changed to identify which power IC to use with OMAP36xx 1 GHz.

www.ti.com

Original device name (VDD1 @ 1.2 A)	New device name (VDD1@ 1.4 A)
TPS65950A2	TPS65950A3
TPS65921B	TPS65921B1

3.2 Specification Update

This section summarizes VDD1 electrical characteristics.

NOTE: Data manuals are the only reference for electrical parameters. Table 3 and Table 4 are for explanation only.

3.2.1 VDD1 Specification for TPS65950A2 and TPS65921B

Parameter	Comments	Min	Тур	Max	Unit
Input voltage range		2.7	3.6	4.5	V
Output voltage		0.6		1.45	V
Output voltage step	Covering the 0.6 to 1.45-V range		12.5		mV
Output accuracy ⁽¹⁾	0.6 to < 0.8 V	-6%		6%	
	0.8 to 1.45 V	-4%		4%	
Switching frequency			3.2		MHz
Conversion efficiency ⁽²⁾ in active and	I _o = 100 mA, sleep		82%		
sleep modes	100 mA < I ₀ < 400 mA		85%		
	400 mA < I ₀ < 600 mA		80%		
	600 mA < I ₀ < 1.1 A		75%		
Output current	Active mode			1.2	А
	Sleep mode			10	mA
Ground current (I _Q)	Off at 30°C			3	μA
	Sleep, unloaded		30	50	
	Active, unloaded, not switching			300	
Short-circuit current	V _{IN} = V _{Max}		2.2		А
DC load regulation	$0 < I_{O} < I_{MAX}$			20	mV
Transient load regulation ⁽³⁾	I_{O} = 10 mA to ($I_{MAX}/2$) + 10 mA, Maximum slew rate is $I_{MAX}/2/100$ ns	-65		50	mV
DC line regulation				10	mV
Transient line regulation	300 mV_{PP} AC input, 10- μs rise and fall time			10	mV
Startup time			0.25	1	ms
Recovery time	From sleep to on mode with constant load		<10	100	μs
Slew rate (rising or falling) ⁽⁴⁾		4	8	16	mV/µs
Output shunt resistor (pulldown)			150		Ω
External coil	Value	0.7	1	1.3	μH
	DCR			0.1	Ω
	Saturation current	1.8			А

Table 3. VDD1 DC-DC Regulator Characteristics

⁽¹⁾ Accuracy includes all variations (line and load regulations, line and load transients, temperature, and process).

⁽²⁾ VBAT = 3.8 V, VDD1 = 1.3 V, Fs = 3.2 MHz, L = 1 μ H, L_{DCR} = 100 mΩ, C = 10 μ F, and ESR = 10 mΩ

 $^{(3)}$ Output voltage must discharge the load current completely and settle to its final value within 100 μ s.

⁽⁴⁾ Load current varies proportionally with the output voltage. The slew rate is for increasing and decreasing voltages and the maximum load current is 1.1 A.



Parameter	Comments	Min	Тур	Max	Unit
External capacitor ⁽⁵⁾	Value	8	10	12	μF
	Equivalent series resistance (ESR) at switching frequency	0		20	mΩ

Table 3. VDD1 DC-DC Regulator Characteristic	s (continued)
--	---------------

⁽⁵⁾ Under current load condition step:

Imax/2 (550 mA) in 100 ns with a \pm 20% external capacitor accuracy or Imax/3 (367 mA) in 100 ns with a \pm 50% external capacitor accuracy

3.2.2 VDD1 Specification for TPS65950A3 and TPS65921B1

Parameters that changed for 1.4-GHz support are in **bold**.

Table 4. VDD1 DC-DC Regulator Characteristics

Parameter	Comments	Min	Тур	Max	Unit
Input voltage range		2.7	3.6	4.5	V
Output voltage		0.6		1.45	V
Output voltage step	Covering the 0.6 to 1.45-V range		12.5		mV
Output accuracy ⁽¹⁾	0.6 to < 0.8 V	-6%		6%	
	0.8 to 1.45 V	-4%		4%	
Switching frequency			3.2		MHz
Conversion efficiency ⁽²⁾ in active	I _o = 100 mA, sleep		82%		
and sleep modes	100 mA < I_0 < 400 mA, active		85%		
	400 mA < I_0 < 600 mA, active		80%		
	600 mA < I _O < 1.1 A, active	ode, output voltage 0.6–1.21.2node, output voltage1.4ode10			
Output current	Active mode, output voltage 0.6–1.2 V			1.2	A
	Active mode, output voltage 1.2–1.45 V			1.4	Α
	Sleep mode			10	mA
Ground current (I _Q)	Off at 30°C			3	μA
	Sleep, unloaded		30	50	μA
	Active, unloaded, not switching			300	μA
Short-circuit current	V _{IN} = V _{Max}		2.2		А
DC load regulation				20	mV
Transient load regulation ⁽³⁾	$I_0 = 10$ mA to 600 mA, Maximum slew rate is 600 mA/100 ns	-65		50	mV
DC line regulation				10	mV
Transient line regulation	300 mV _{PP} AC input 10-µs rise and fall time			10	mV
Startup time			0.25	1	ms
Recovery time	From sleep to on mode with constant load		<10	100	μs
Slew rate (rising or falling) ⁽⁴⁾		4	8	16	mV/µs
Output shunt resistor (pull down)			150		Ω
External coil	Value	0.7	1	1.3	μH
	DCR			0.1	Ω
	Saturation current	2.1			Α

⁽¹⁾ Accuracy includes all variations (line and load regulations, line and load transients, temperature, and process).

⁽²⁾ **VBAT = 3.6 V, VDD1 = 1.2 V**, Fs = 3.2 MHz, L, C according to specification

⁽³⁾ Output voltage must discharge the load current completely and settle to its final value within 100 µs.

⁽⁴⁾ Load current varies proportionally with the output voltage. The slew rate is for increasing and decreasing voltages and the maximum load current is 1.1 A.



www.ti.com

	•		•		
Parameter Comments		Min	Тур	Max	Unit
External capacitor	Value (two capacitors of 22 µF in parallel are recommended)		44		μF
	ESR at switching frequency	0		20	mΩ

Table 4. VDD1 DC-DC Regulator Characteristics (continued)

5

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Audio	www.ti.com/audio	Communications and Telecom	www.ti.com/communications
Amplifiers	amplifier.ti.com	Computers and Peripherals	www.ti.com/computers
Data Converters	dataconverter.ti.com	Consumer Electronics	www.ti.com/consumer-apps
DLP® Products	www.dlp.com	Energy and Lighting	www.ti.com/energy
DSP	dsp.ti.com	Industrial	www.ti.com/industrial
Clocks and Timers	www.ti.com/clocks	Medical	www.ti.com/medical
Interface	interface.ti.com	Security	www.ti.com/security
Logic	logic.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Power Mgmt	power.ti.com	Transportation and Automotive	www.ti.com/automotive
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com	Wireless	www.ti.com/wireless-apps
RF/IF and ZigBee® Solutions	www.ti.com/lprf		

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2011, Texas Instruments Incorporated