

PMP4494 REV A Bill of Materials

Designator	Quantity	Value	PartNumber	Manufacturer	Description	PackageReference
C1, C16, C17,	4	4.7uF	12063D475KAT2A	AVX	CAP, CERM, 4.7 µF, 25 V, +/- 10%, X5R, 1206	1206
C18						
C2, C3, C4, C5,	12	470uF	8.6508045702e+011	Wurth Elektronik	CAP, AL, 470 μF, 25 V, +/- 20%, 0.15 ohm, SMD	D10xL10.5mm
C6, C7, C8, C9,						
C10, C11, C12,						
C13						
C14	1	0.01uF	C0603C103J5RACTU	Kemet	CAP, CERM, 0.01 µF, 50 V, +/- 5%, X7R, 0603	0603
C15, C19, C23,	6	0.1uF	06033C104JAT2A	AVX	CAP, CERM, 0.1 µF, 25 V, +/- 5%, X7R, 0603	0603
C28, C29, C32						
C20	1	100uF	C1210C107M9PACTU	Kemet	CAP, CERM, 100 μF, 6.3 V, +/- 20%, X5R, 1210	1210
C21, C25	2	1uF	GRM188R61E105KA12D	MuRata	CAP, CERM, 1uF, 25V, +10/%, X5R, 0603	0603
C22	1	4700pF	06031C472JAT2A	AVX	CAP, CERM, 4700 pF, 100 V, +/- 5%, X7R, 0603	0603
C24	1	120pF	06035A121JAT2A	AVX	CAP, CERM, 120 pF, 50 V, +/- 5%, C0G/NP0, 0603	0603
C30	1	10uF	GRM31CR61E106KA12L	MuRata	CAP, CERM, 10 µF, 25 V, +/- 10%, X5R, 1206	1206
C31	1	47pF	GRM1885C1H470JA01D	MuRata	CAP, CERM, 47 pF, 50 V, +/- 5%, C0G/NP0, 0603	0603
C33	1	100uF	EEE-FC1C101P	Panasonic	CAP, AL, 100 µF, 16 V, +/- 20%, 0.4 ohm, SMD	SMT Radial E
C34	1	100uF	EEE-FC1A101P	Panasonic	CAP, AL, 100 µF, 10 V, +/- 20%, 0.4 ohm, SMD	SMT Radial E
D1	1	30V	MBR130LSFT1G	ON Semiconductor	Diode, Schottky, 30 V, 1 A, SOD-123FL	SOD-123FL
J2	1		ED555/2DS	On-Shore Technology	Terminal Block, 6A, 3.5mm Pitch, 2-Pos, TH	7.0x8.2x6.5mm
L1	1	22uH	74437324220	Wurth Elektronik	Inductor, Shielded Drum Core, Powdered Iron, 22 µH, 1 A, 0.47 ohm, SMD	4.45x1.8x4.06mm
L2	1	15uH	74437349150	Wurth Elektronik	Inductor, Shielded Drum Core, Ferrite, 15 µH, 1.7 A, 0.066 ohm, SMD	7050
Q1, Q2	2	-30V	SI2343CDS-T1-GE3	Vishay-Siliconix	MOSFET, P-CH, -30 V, -5.9 A, SOT-23	SOT-23
Q3, Q4, Q5	3	60V	2N7002-7-F	Diodes Inc.	MOSFET, N-CH, 60 V, 0.17 A, SOT-23	SOT-23
R1, R2, R7	3	10.0k	CRCW060310K0FKEA	Vishay-Dale	RES, 10.0 k, 1%, 0.1 W, 0603	0603
R3	1	150k	CRCW0603150KFKEA	Vishay-Dale	RES, 150 k, 1%, 0.1 W, 0603	0603
R4	1	0	CRCW06030000Z0EA	Vishay-Dale	RES, 0, 5%, 0.1 W, 0603	0603
R5	1	130k	CRCW0603130KFKEA	Vishay-Dale	RES, 130 k, 1%, 0.1 W, 0603	0603
R6	1	31.6k	CRCW060331K6FKEA	Vishay-Dale	RES, 31.6 k, 1%, 0.1 W, 0603	0603
R8	1	200k	RC0603FR-07200KL	Yageo America	RES, 200 k, 1%, 0.1 W, 0603	0603
R9	1	10.0k	CRCW060310K0FKEA	Vishay-Dale	RES, 10.0k ohm, 1%, 0.1W, 0603	0603
R10	1	12.1k	CRCW060312K1FKEA	Vishay-Dale	RES, 12.1 k, 1%, 0.1 W, 0603	0603
R12, R15	2	51.0	RC0603FR-0751RL	Yageo America	RES, 51.0, 1%, 0.1 W, 0603	0603
R13	1	47	PNP300JR-73-100R	Yageo America	RES, 100, 5%, 3 W, TH	3W Axial resistor
R16	1	4.70k	RC0603FR-074K7L	Yageo America	RES, 4.70 k, 1%, 0.1 W, 0603	0603
R17, R18, R20,	4	10.0k	RC0603FR-0710KL	Yageo America	RES, 10.0 k, 1%, 0.1 W, 0603	0603
R21						
R19	1	120k	RC0603FR-07120KL	Yageo America	RES, 120 k, 1%, 0.1 W, 0603	0603
R23	1	240k	RC0603FR-07240KL	Yageo America	RES, 240 k, 1%, 0.1 W, 0603	0603
U1	1		TPS61170DRV	Texas Instruments	1.2A High Voltage Boost Converter in 2x2mm QFN Package, DRV0006A	DRV0006A
U2	1		LM20242MH	Texas Instruments	36V, 2A PowerWise Adjustable Frequency Synchronous Buck Regulator,	MXA20A
					20-pin TSSOP-EP	
U3	1	1	TLV809I50DBZR	Texas Instruments		DBZ0003A
U.3						

Designator	Quantity	Value	PartNumber	Manufacturer	Description	PackageReference
C26, C27	0	0.01uF	C0603C103J5RACTU	Kemet	CAP, CERM, 0.01 µF, 50 V, +/- 5%, X7R, 0603	0603
R11, R14	0	150k	CRCW0603150KFKEA	Vishay-Dale	RES, 150 k, 1%, 0.1 W, 0603	0603
R22	0	31.6k	CRCW060331K6FKEA	Vishay-Dale	RES, 31.6 k, 1%, 0.1 W, 0603	0603

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ('TI') reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

TI's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

TI's standard terms of sale for semiconductor products (<u>http://www.ti.com/sc/docs/stdterms.htm</u>) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's noncompliance with the terms and provisions of this Notice.

> Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2016, Texas Instruments Incorporated