

These tests were performed with the Coilcraft NA6111-AL transformer.


Efficiency and Regulation

				<b>J3</b>	<b>J3</b>	<b>J3</b>	
<b>Iout</b>	<b>Vout</b>	<b>Iout</b>	<b>Vout</b>	<b>Iin</b>	<b>Vin</b>	<b>Eff</b>	
2.00	3.329	1.00	5.064	0.3772	36.00	86.3%	
2.00	3.329	0.50	5.086	0.2942	36.00	86.9%	
2.00	3.329	0.00	5.108	0.2136	36.00	86.6%	
0.00	3.331	1.00	4.945	0.1573	36.00	87.3%	
0.00	3.331	0.00	4.989	0.0098	36.00	0.0%	
1.00	3.330	0.50	5.025	0.1848	36.00	87.8%	
1.00	3.330	1.00	5.003	0.2637	36.00	87.8%	
				<b>J3</b>	<b>J3</b>	<b>J3</b>	
<b>Iout</b>	<b>Vout</b>	<b>Iout</b>	<b>Vout</b>	<b>Iin</b>	<b>Vin</b>	<b>Eff</b>	
2.00	3.329	1.00	5.051	0.2754	48.00	88.6%	
2.00	3.329	0.50	5.069	0.2163	48.00	88.5%	
2.00	3.329	0.00	5.088	0.1585	48.00	87.5%	
0.00	3.331	1.00	4.951	0.1178	48.00	87.6%	
0.00	3.331	0.00	4.987	0.0094	48.00	0.0%	
1.00	3.330	0.50	5.018	0.1378	48.00	88.3%	
1.00	3.330	1.00	5.000	0.1948	48.00	89.1%	
				<b>J3</b>	<b>J3</b>	<b>J3</b>	
<b>Iout</b>	<b>Vout</b>	<b>Iout</b>	<b>Vout</b>	<b>Iin</b>	<b>Vin</b>	<b>Eff</b>	
2.00	3.329	1.00	5.045	0.2303	57.00	89.2%	
2.00	3.329	0.50	5.062	0.1815	57.00	88.8%	
2.00	3.329	0.00	5.079	0.1337	57.00	87.4%	
0.00	3.331	1.00	4.953	0.1001	57.00	86.8%	
0.00	3.331	0.00	4.987	0.0095	57.00	0.0%	
1.00	3.330	0.50	5.015	0.1166	57.00	87.8%	
1.00	3.330	1.00	4.999	0.1639	57.00	89.2%	
<b>Max Load Efficiency without bridge</b>							
<b>Iout</b>	<b>Vout</b>	<b>Iout</b>	<b>Vout</b>	<b>Iin</b>	<b>Vin</b>	<b>Eff</b>	
2.00	3.329	1.00	5.064	0.3772	34.16	91.0%	36.0V at J3
2.00	3.329	1.00	5.051	0.2754	46.21	92.0%	48.0V at J3
2.00	3.329	1.00	5.045	0.2303	55.28	91.9%	57.0V at J3
Vin measured at FB1/FB2							


**Ripple and Noise**

48V input; 3.3V/2A, 5V/1A loads; 20MHz BWL.

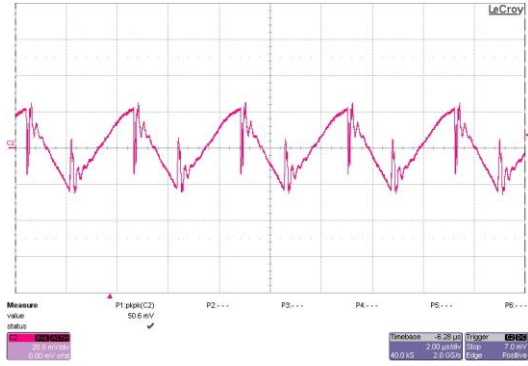
3.3V Output Ripple (C22), 20mV/div  
Measured 50.6mV peak to peak:



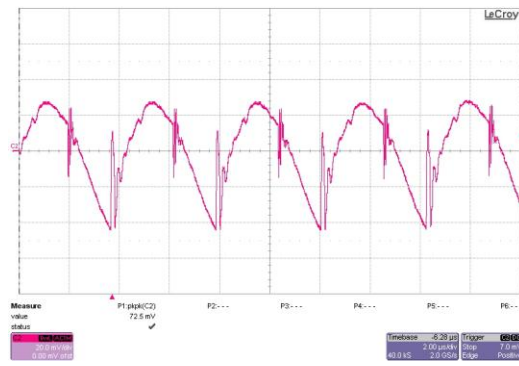5V Output Ripple (C14), 20mV/div  
Measured 72.5mV peak to peak:




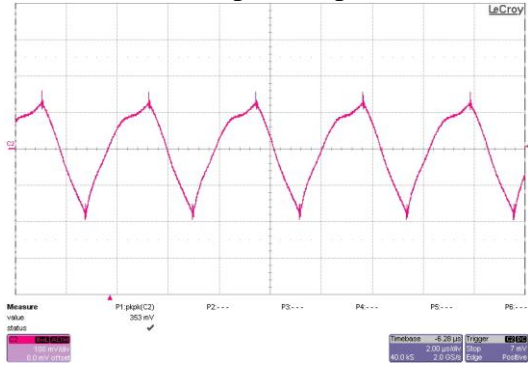Input Ripple (C15), 100mV/div  
Measured 353mV peak to peak:




**Turn On Response**

48VIN, Max Loads, 1msec/div:

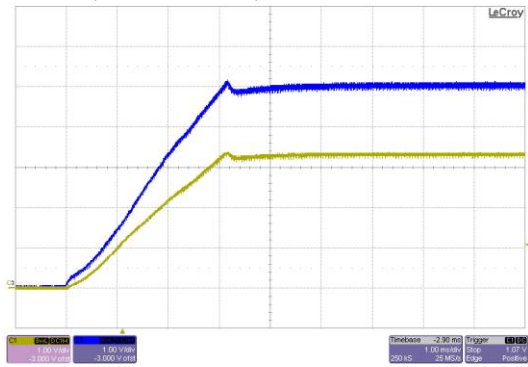


48VIN, 0A Loads, 1msec/div:

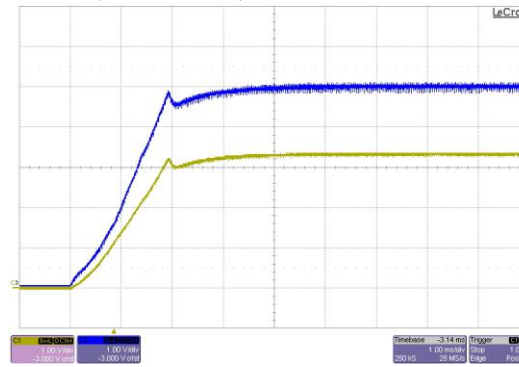

Top, 5V output, 1V/div; Bottom, 3.3V output, 1V/div

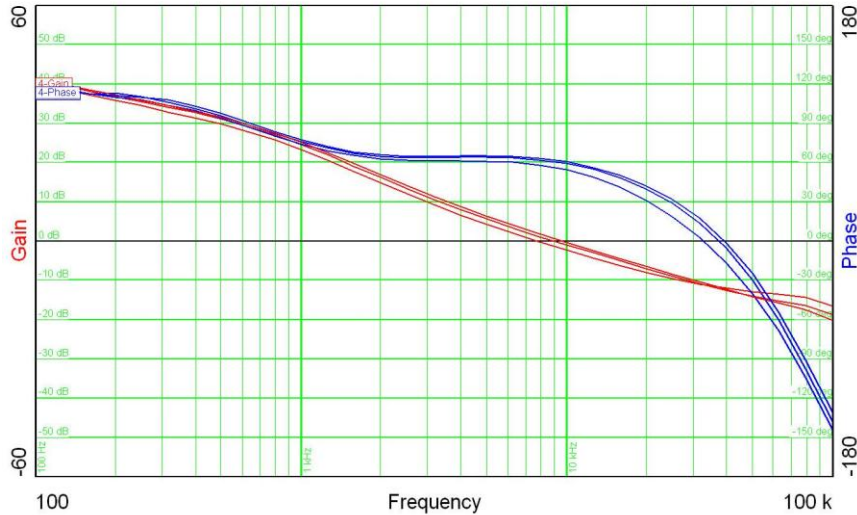**Loop Stability**

The measured Bode plot of the converter is shown below.



<b>Vin</b>	<b>BW</b>	<b>PM</b>	<b>GM</b>
<b>Volts</b>	<b>KHz</b>	<b>Deg</b>	<b>dB</b>
36.00	7.7	58.0	11.1
48.00	8.9	60.0	12.1
57.00	9.7	60.0	12.2

**Dynamic Loading**

One output was pulsed. The output not being pulsed was loaded to its max value.


**36V INPUT**

**3.3V load step, 200mA to 1A:**

3.3V Response

50mV/div, 1msec/div


Measured 83mV peak to peak:

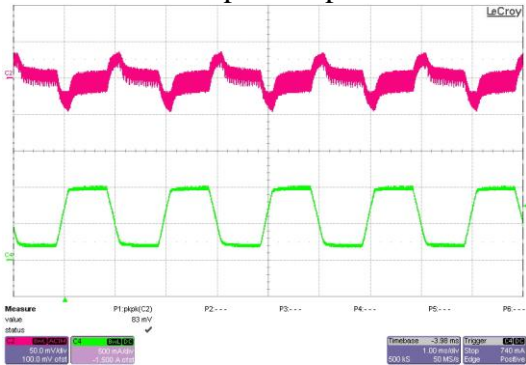

5V Response

50mV/div

Measured 148mV peak to peak:

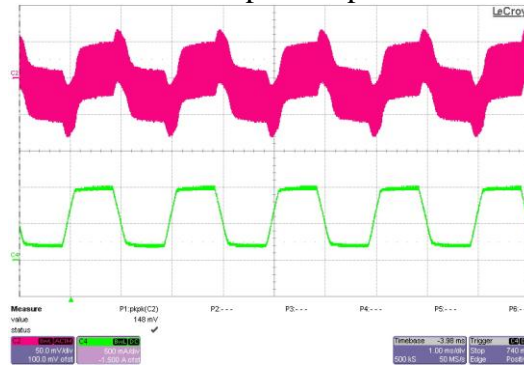

**3.3V load step, 1A to 2A:**

3.3V Response

50mV/div, 1msec/div


Measured 108mV peak to peak:



5V Response

50mV/div

Measured 161mV peak to peak:

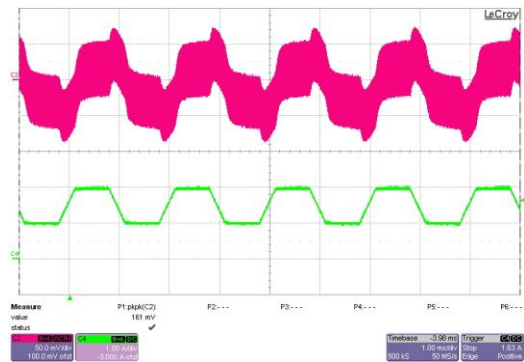


**5V load step, 100mA to 500mA:**

3.3V Response

50mV/div, 1msec/div


Measured 123mV peak to peak:

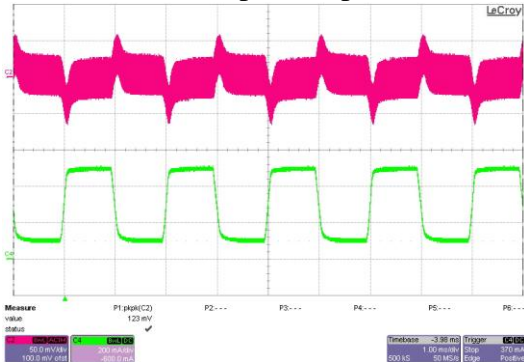

5V Response

50mV/div

Measured 164mV peak to peak:

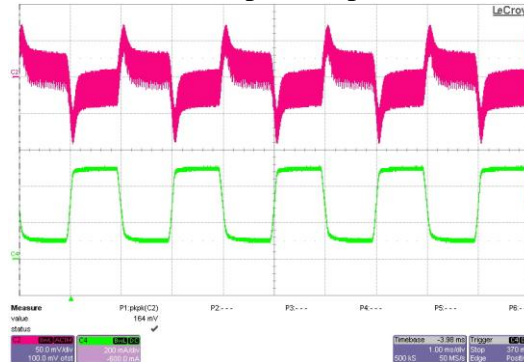


**5V load step, 500mA to 1A:**

3.3V Response

50mV/div, 1msec/div


Measured 134mV peak to peak:

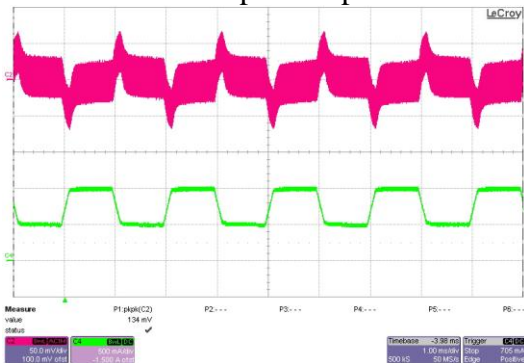

5V Response

50mV/div

Measured 203mV peak to peak:

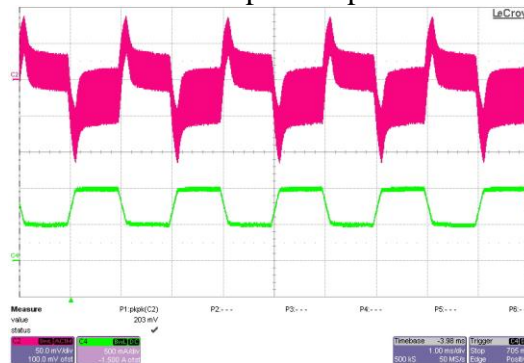


**48V INPUT**

**3.3V load step, 1A to 2A:**

3.3V Response

50mV/div, 1msec/div


Measured 92mV peak to peak:

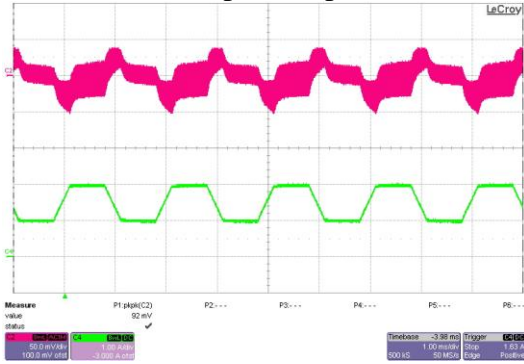

5V Response

50mV/div

Measured 144mV peak to peak:

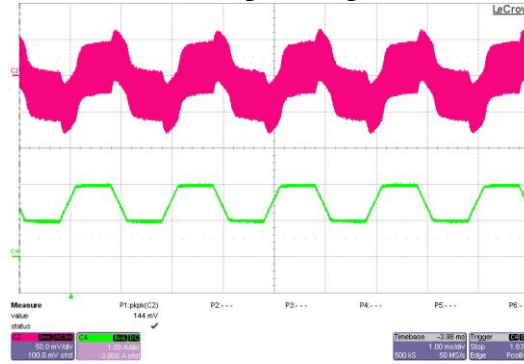


**5V load step, 500mA to 1A:**

3.3V Response

50mV/div, 1msec/div


Measured 113mV peak to peak:

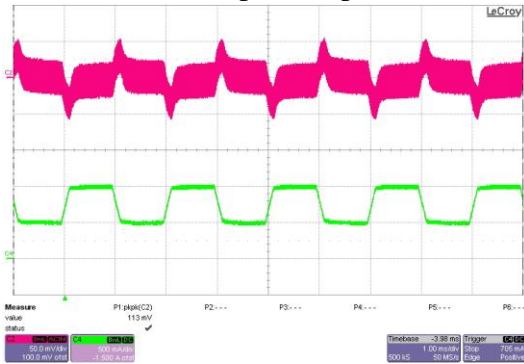


5V Response

50mV/div

Measured 178mV peak to peak:

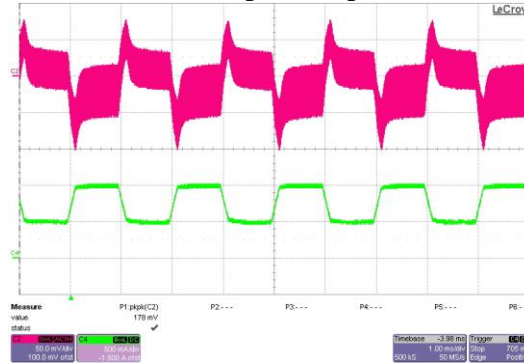

**Photo**

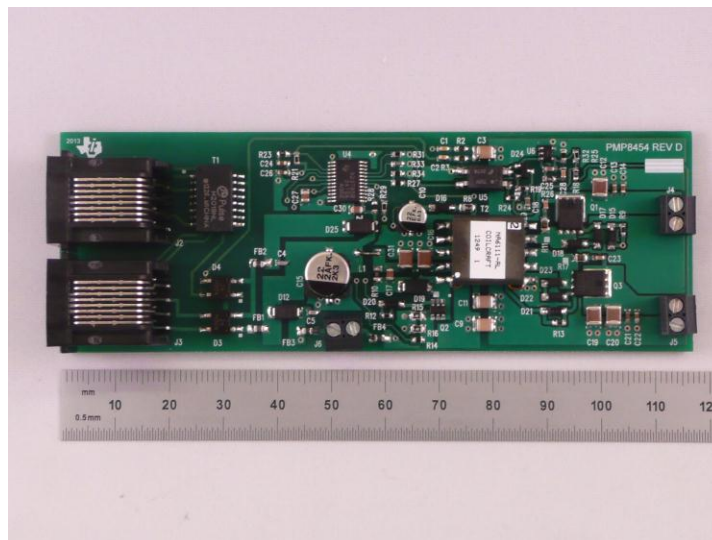

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated